

CSS351 Assignment

Name: Arunopal Chakraborty

Roll No.: 20CS8058

1. Design full adder using half adder.

Theory:

If we draw the truth table of the full adder, we will get:

A	B	C	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

On doing its K-map simplification, we will get:

$$\text{Sum} = (A \oplus B \oplus C)$$


$$\text{Carry} = (A \oplus B).C + A.B$$

Now for a half adder, we have:

$$\text{Sum} = (A \oplus B)$$

$$\text{Carry} = A.B$$

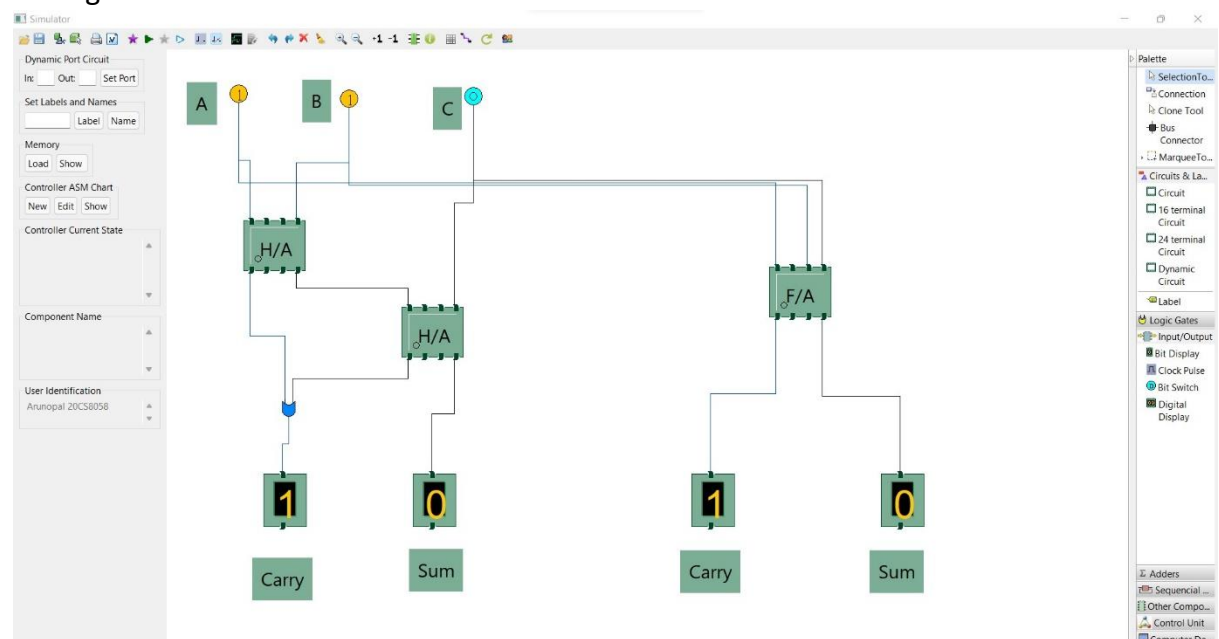Thus for a full adder, we need 2 half-adders such that, we are adding A and B in one and adding its result with C in 2nd half adder.



2. Design a 4 bit CLA using basic logic gates.

Theory:

In ripple carry adder (RCA) the delay is added from beginning to last. So, the total gate delay increases a lot. To reduce this we will use the Carry Look Ahead Adder (CLA).

If we denote $P_i = A_i \oplus B_i$

and $G_i = A_i \cdot B_i$

We will get sum, $S_i = P_i \oplus C_i$

and carry-out, $C_{i+1} = G_i + P_i \cdot C_i$

Thus, we can derive,

$$C_1 = G_0 + P_0 \cdot C_0$$

$$C_2 = G_1 + P_1 \cdot C_1 = G_1 + P_1 \cdot (G_0 + P_0 \cdot C_0)$$

$$= G_1 + P_1 \cdot G_0 + P_1 \cdot P_0 \cdot C_0$$


$$C_3 = G_2 + P_2 \cdot C_2 = G_2 + P_2 \cdot (G_1 + P_1 \cdot G_0 + P_1 \cdot P_0 \cdot C_0)$$

$$= G_2 + P_2 \cdot G_1 + P_2 \cdot P_1 \cdot G_0 + P_2 \cdot P_1 \cdot P_0 \cdot C_0$$

$$C_4 = G_3 + P_3 \cdot C_3 = G_3 + P_3 \cdot (G_2 + P_2 \cdot G_1 + P_2 \cdot P_1 \cdot G_0 + P_2 \cdot P_1 \cdot P_0 \cdot C_0)$$

$$= G_3 + P_3 \cdot G_2 + P_3 \cdot P_2 \cdot G_1 + P_3 \cdot P_2 \cdot P_1 \cdot G_0 + P_3 \cdot P_2 \cdot P_1 \cdot P_0 \cdot C_0$$

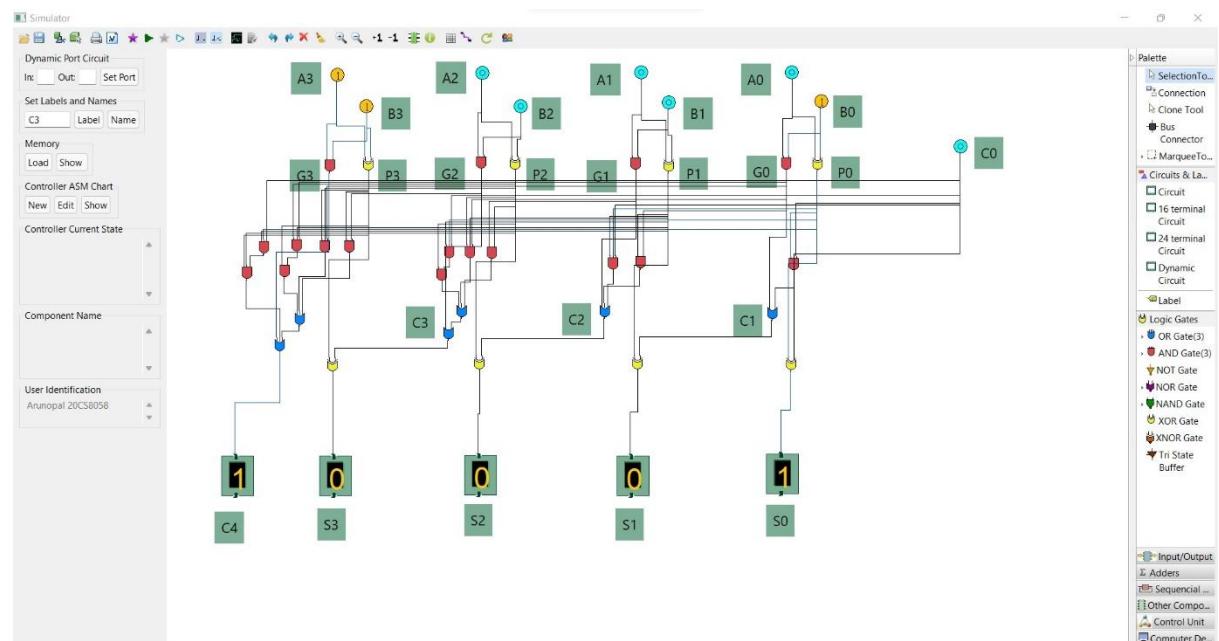This will significantly reduce the gate delay by making C_4 to be affected by only 2 stages of gate delays, namely, and-gates and or-gates.



3. Convert:


a) SR flip-flop to JK flip-flop.

Truth table:


J	K	Q(t)	Q(t+1)	S	R
0	0	0	0	0	X

0	0	1	1	X	0
0	1	0	0	0	X
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	1	X	0
1	1	0	1	1	0
1	1	1	0	0	1

 
Using K-map we get $S = JQ'$ and $R = KQ$.



Simulator:

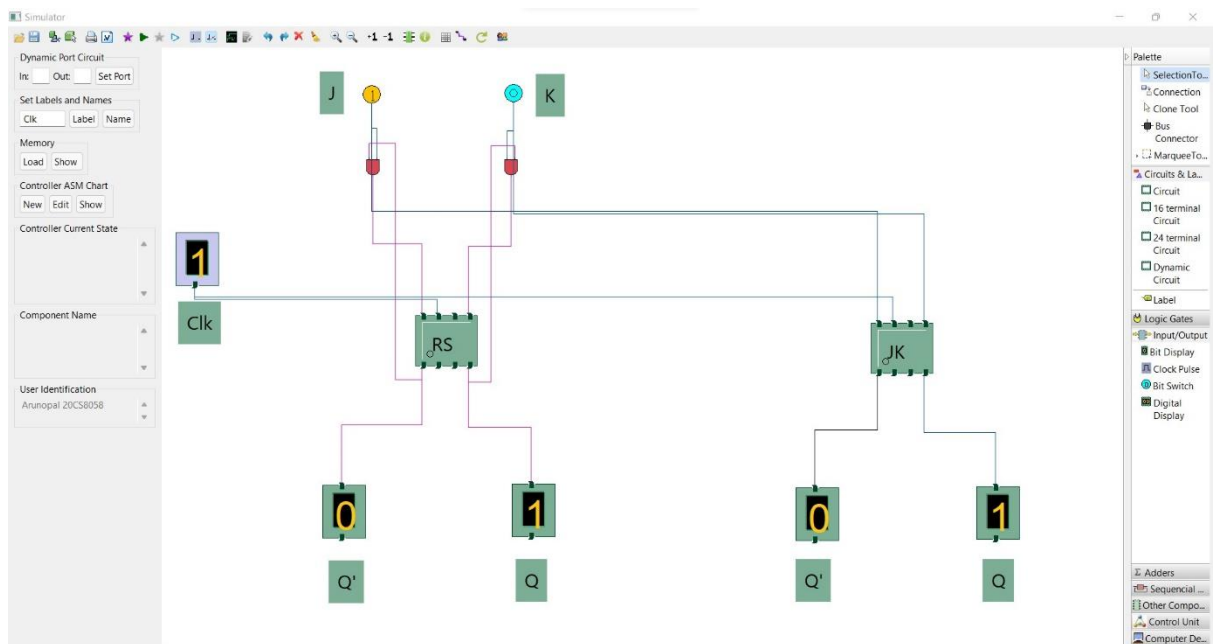

Waveform:

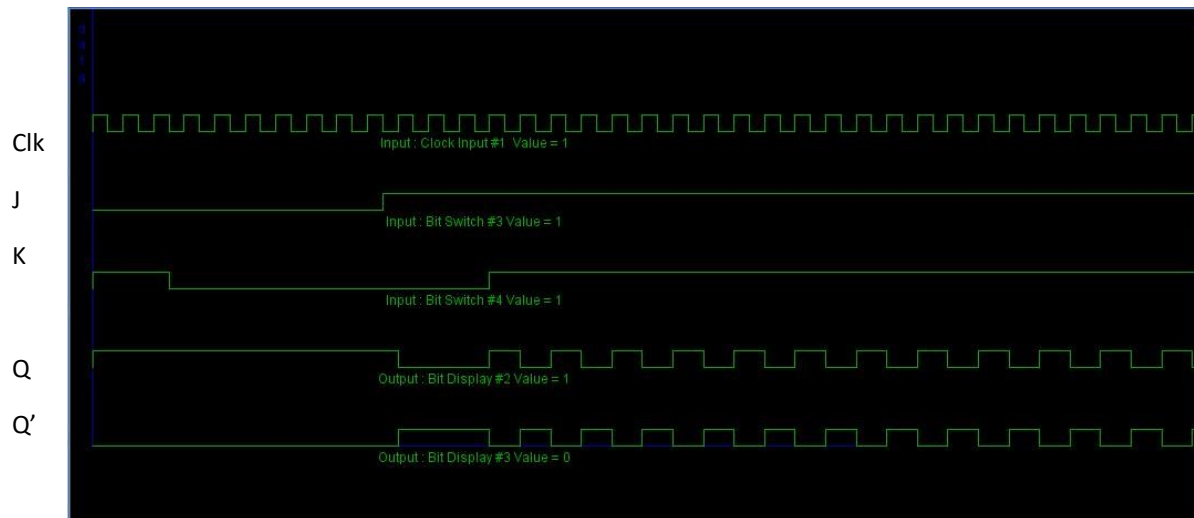


b) SR flip-flop to D flip-flop.


Truth table:

D	Q(t)	Q(t+1)	S	R
0	0	0	0	X
0	1	0	0	1
1	0	1	1	0
1	1	1	X	0

From K-map we get $S = D$ and $R = D'$.

 

Simulator:

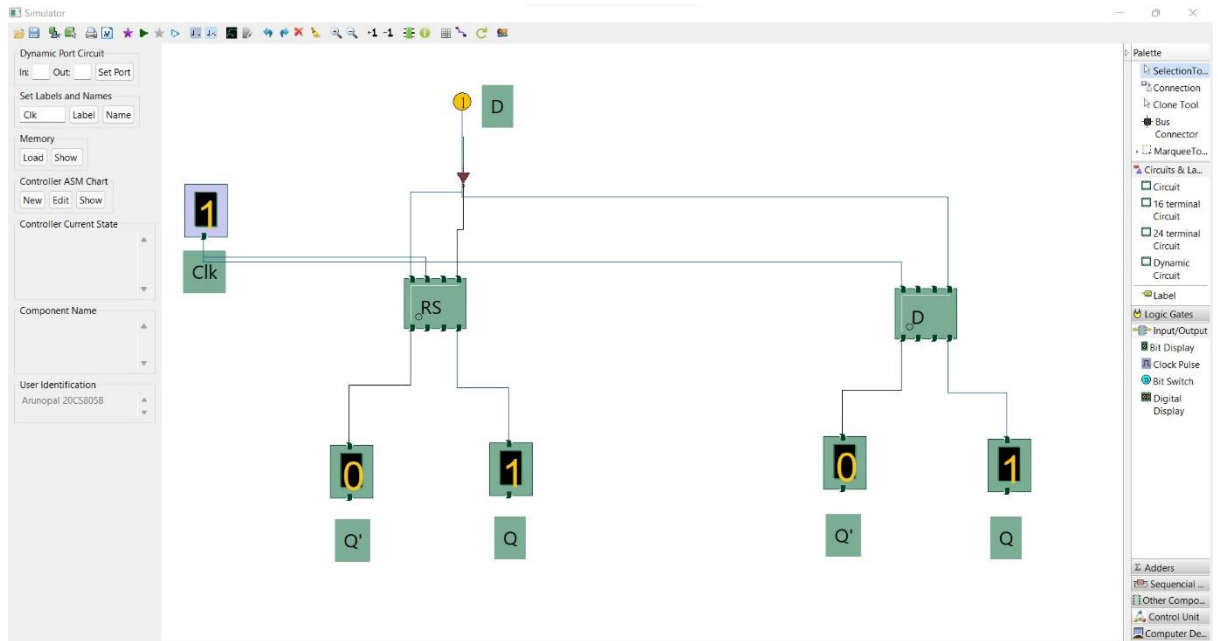

Waveform:

